

Name: \_\_\_\_\_ Date: \_\_\_\_\_



## Switches

Draw the switch ON

Draw the switch OFF

Which parts of the switch CONDUCT electricity?

---

Challenge: Why are switches important?

Extension: Can you draw a circuit diagram using electrical symbols to show your switch 'on' and 'off'?

